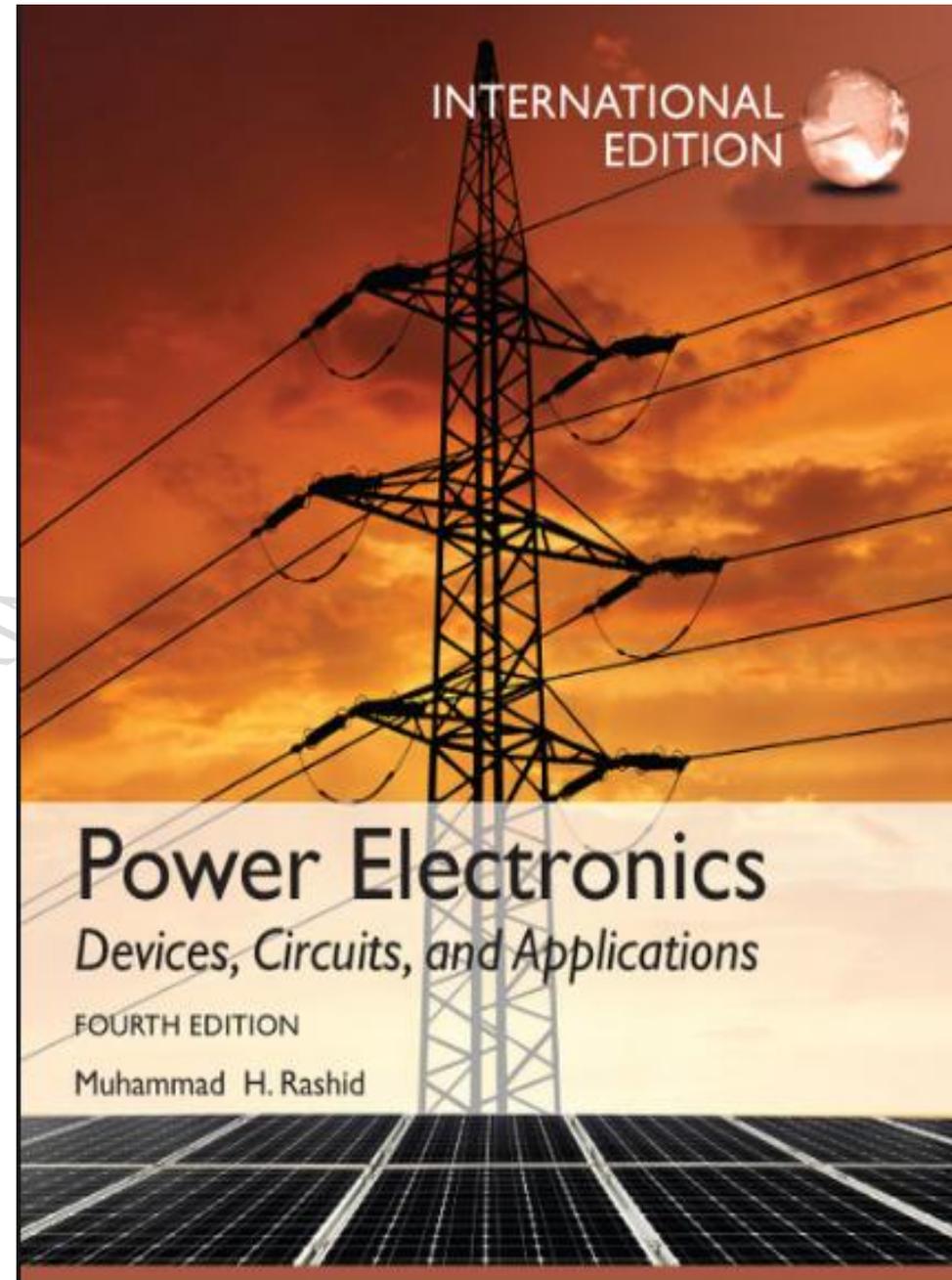


**University of Technology**  
**Laser and Optoelectronic Engineering**  
**Department**  
**Power Electronics/2018-2019)**  
**For the third years (Laser Engineering)**

**Prepared by: Lec. Dr. Mothana Amaar Hassan**  
**Laser and Optoelectronic Engineering**  
**Department**




***Ref: Power Electronics 4<sup>th</sup> edition/ Muhammed H. Rashid***


# Lecture No. 6
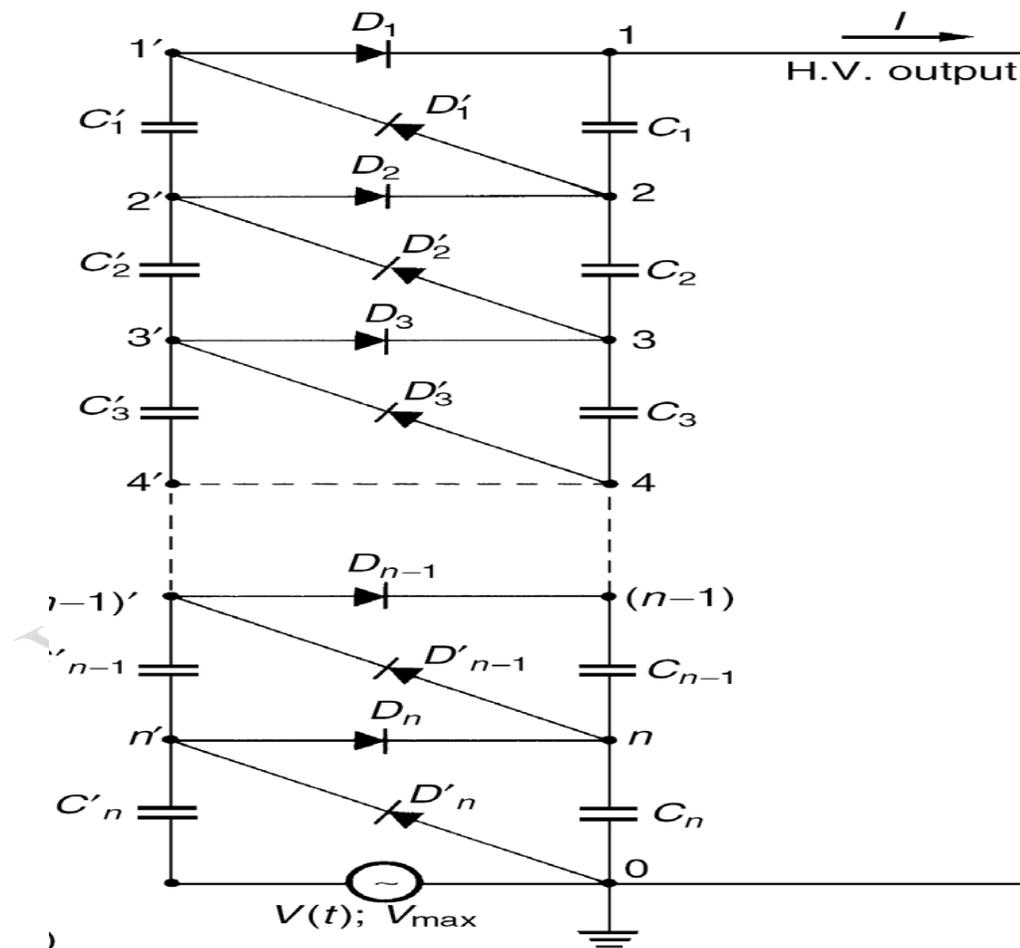
## Cascade Voltage Multiplier

To demonstrate the principle only, an n-stage single-phase cascade circuit of the 'Cockcroft-Walton type', shown in figure below, will be presented.



**HV output open-circuited:  $I = 0$ .** The portion (0 - n' - V(t)) is a half-wave rectifier circuit in which  $C'_n$  charges up to a voltage of  $+V_{max}$  if  $V(t)$  has reached the lowest potential,  $-V_{max}$ . If  $C'_n$  is still uncharged, the rectifier  $D_n$  conducts as soon as  $V(t)$  increases. As the potential of point n' swings up to  $+V_{2max}$  during the period  $T = 1/f$ , point n attains further on a steady potential of  $+2V_{max}$  if  $V(t)$  has reached the highest potential of  $+V_{max}$ . The part (n' - n - 0) is therefore a half-wave rectifier, in which the voltage across  $D'_n$  can be assumed to be the a.c. voltage source.

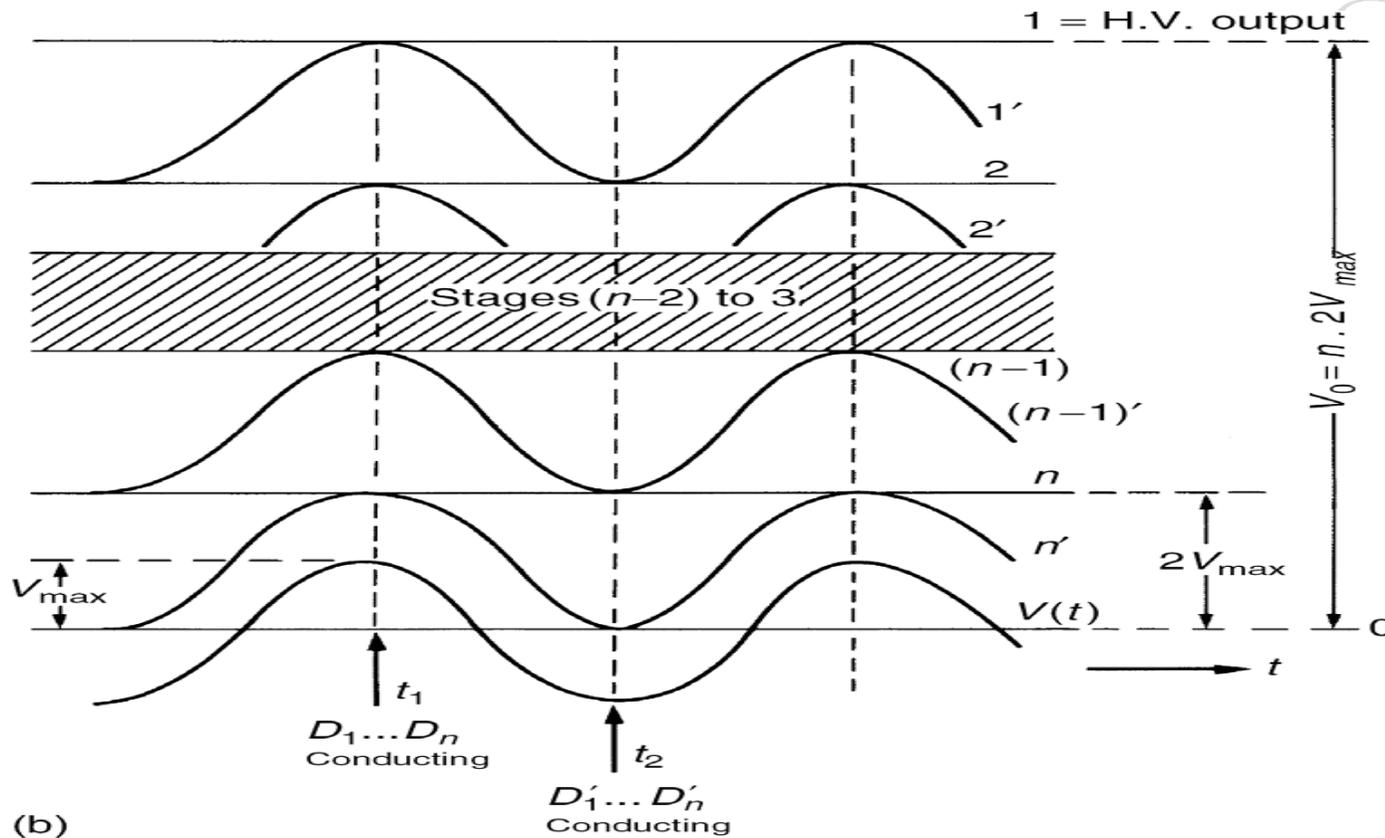


The current through  $D_n$  that charged the capacitor  $C_n$  was not provided by  $D'_n$ , but from  $V(t)$  and  $C'_n$ . We can assume that the voltage across  $C_n$  is not reduced if the potential n' oscillates between zero and  $+2V_{max}$ . If the potential of n', however, is zero, the capacitor  $C'_{n-1}$  is also charged to the

potential of  $n$ , i.e. to a voltage of  $+2V_{\max}$ . The next voltage oscillation of  $V(t)$  from  $-V_{\max}$  to  $+V_{\max}$  will force the diode  $D_{n-1}$  to conduct, so that also  $C_{n-1}$  will be charged to a voltage of  $+2V_{\max}$ .

The steady state potentials at all nodes of the circuit are sketched for the circuit for zero load conditions. From this it can be seen, that:

- 1 The potentials at the nodes ( $1', 2' \dots n'$ ) are oscillating due to the voltage oscillation of  $V(t)$ ;
- 2 The potentials at the nodes ( $1, 2 \dots n$ ) remain constant with reference to ground potential;
- 3 The voltages across all capacitors are of d.c. type, the magnitude of which is  $2V_{\max}$  across each capacitor stage, except the capacitor  $C_n$  which is stressed with  $V_{\max}$  only;
- 4 Every rectifier  $D_1, D'_1 \dots D_n, D'_n$  is stressed with  $2V_{\max}$  or twice a.c. peak voltage; and
- 5 The HV output will reach a maximum voltage of  $2nV_{\max}$ .

**H.V. output loaded:  $I > 0$ .** If the generator supplies any load current  $I$ , the output voltage will never reach the value  $2nV_{\max}$ . There will also be a ripple on the voltage, and therefore we have to deal with two quantities: the voltage drop  $\Delta V_o$  and the peak-to-peak ripple  $2\delta V$ . The sketch in figure below shows the shape of the output voltage and the definitions of  $\Delta V_o$  and  $2\delta V$ .

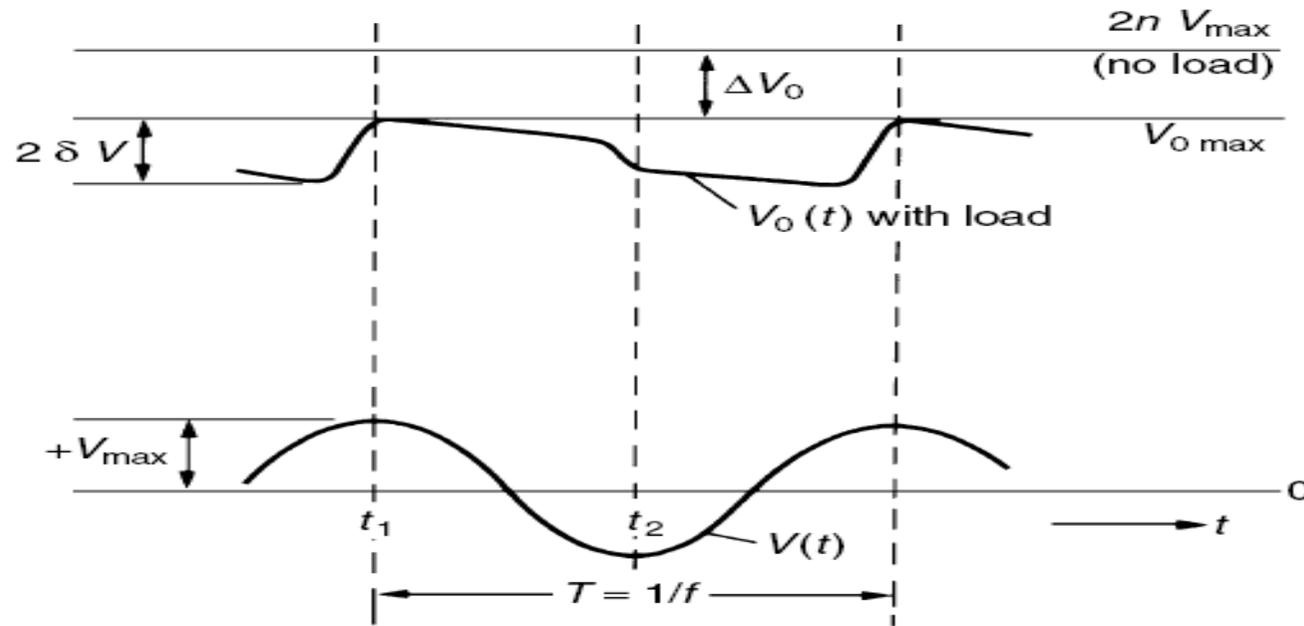

Let a charge  $q$  be transferred to the load per cycle, which is obviously  $q = I \times T$ . This charge comes from the smoothing column, the series connection of  $C_1 \dots C_n$ . If no charge would be transferred during  $T$  from this stack via  $D'_1 \dots D'_n$  to the oscillating column. However, just before the time instant  $t_2$  every diode  $D'_1 \dots D'_n$  transfers the same charge  $q$ , and each of these charges discharges all capacitors on the smoothing column between the relevant node and ground potential, the ripple will be:

$$\delta v = \frac{I}{2f} \left( \frac{1}{C_1} + \frac{2}{C_2} + \frac{3}{C_3} + \dots + \frac{n}{C_n} \right)$$

Thus in a cascade multiplier the lowest capacitors are responsible for most ripple and it would be desirable to increase the capacitance in the lower stages. This is, however, very inconvenient for H.V. cascades, as a voltage breakdown at the load would completely overstress the smaller capacitors within the column. Therefore, equal capacitance values are usually provided, and with  $C = C_1 = C_2 = C_3 \dots C_n$ ,

$$\delta V = \frac{I}{fC} \times \frac{n(n+1)}{4}$$

To calculate the total voltage drop  $\Delta V_o$ , we will first consider the stage  $n$ . Although the capacitor  $C'_n$  at time  $t_1$  will be charged up to the full voltage  $V_{\max}$ , if ideal rectifiers and no voltage drop within the a.c.-source are assumed,

$$\Delta V_o = \frac{I}{fC} \left( \frac{2n^3}{3} + \frac{n^2}{2} - \frac{n}{6} \right)$$

For a given number of stages, this maximum voltage or also the mean value  $V_o = V_{o\max} - \delta V$  will decrease linearly with the load current  $I$  at constant

Where  $V_{o\max} = 2nV_{\max} - \Delta V_o$

LASER ENGINEERING BRANCH