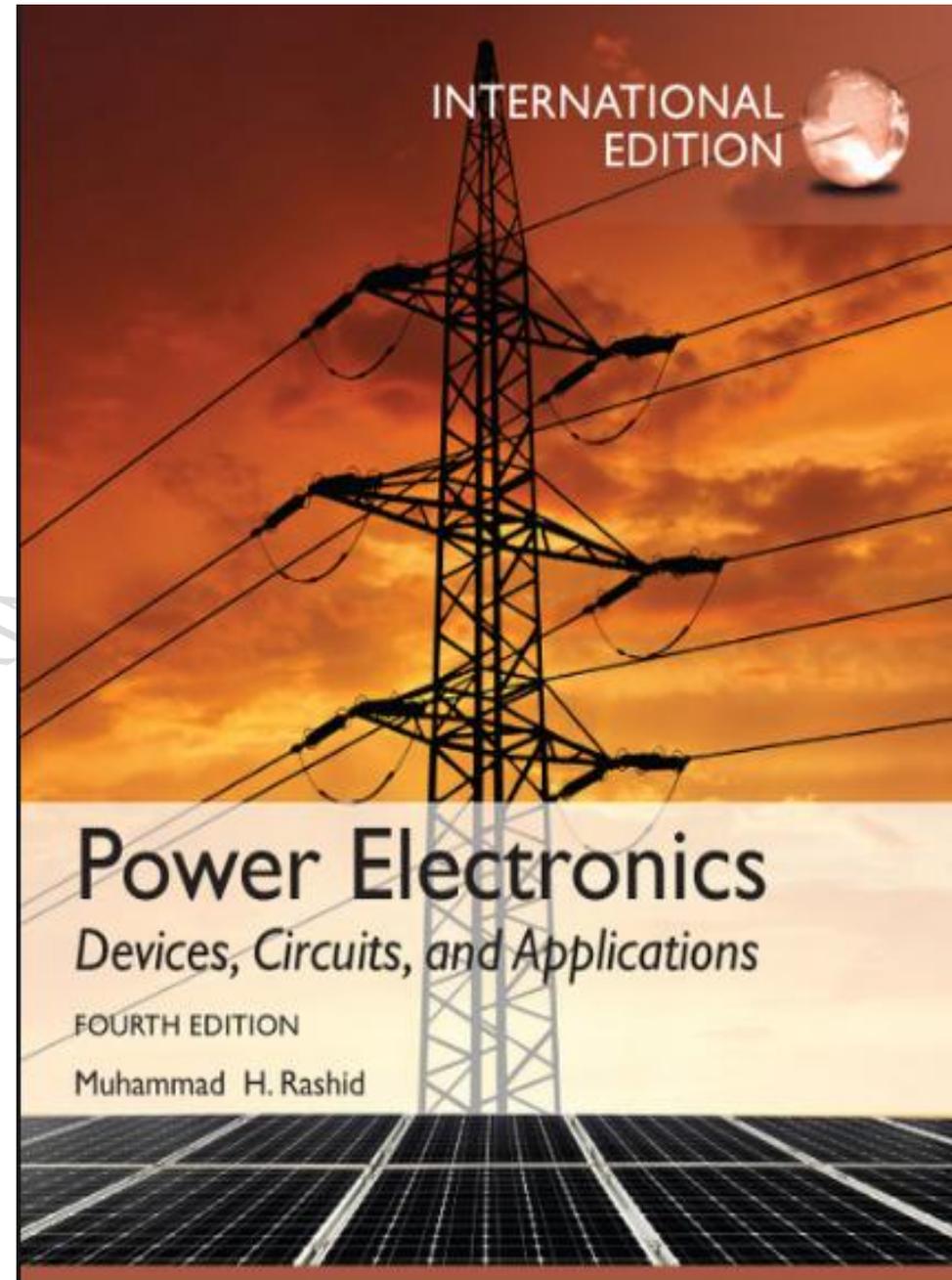


**University of Technology**  
**Laser and Optoelectronic Engineering**  
**Department**  
**Power Electronics/2018-2019)**  
**For the third years (Laser Engineering)**

**Prepared by: Lec. Dr. Mothana Amaar Hassan**  
**Laser and Optoelectronic Engineering**  
**Department**



***Ref: Power Electronics 4<sup>th</sup> edition/ Muhammed H. Rashid***



## Lecture No.7

### Single-Phase Full-Wave Rectifiers

There are two types of single-phase full-wave rectifier, namely, full-wave rectifiers with center-tapped transformer and bridge rectifiers.
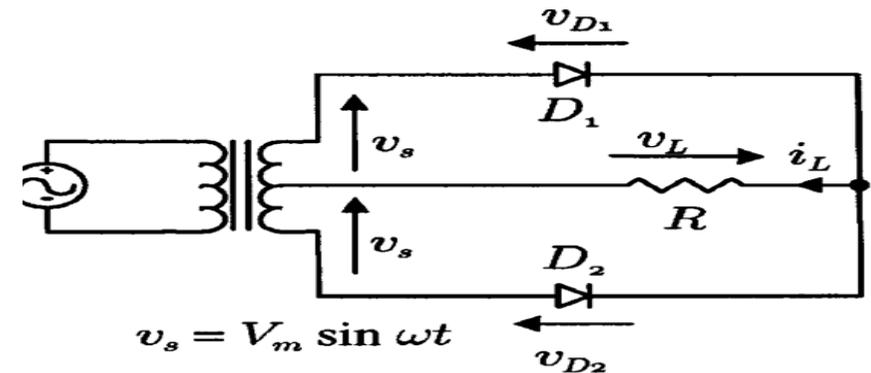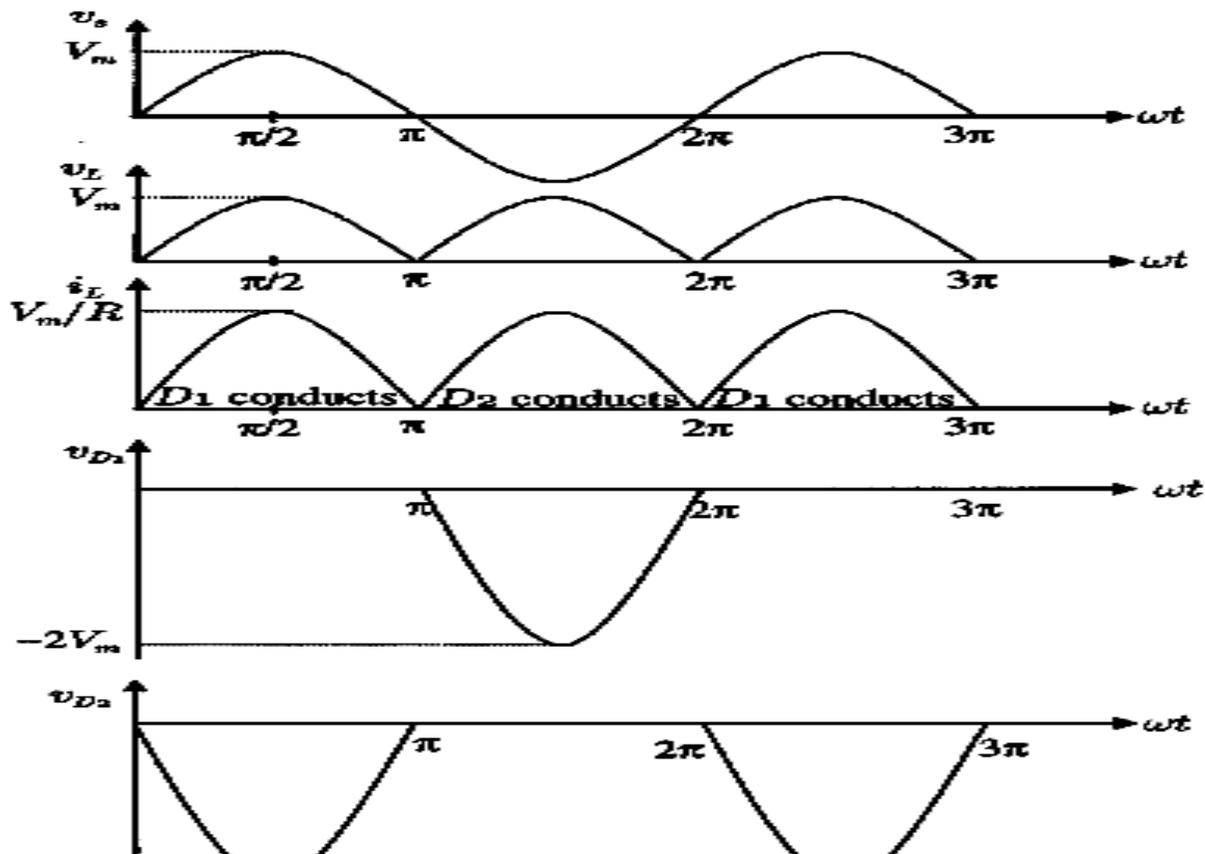
#### *I. full-wave rectifier with a center-tapped transformer:*

It is clear that each diode, together with the associated half of the transformer, acts as a half-wave rectifier. The outputs of the two half-wave rectifiers are combining to produce full-wave rectification in the load.





→It is clear that the peak inverse voltage (PIV) of the diodes is equal to  $2V_m$  during their blocking state.

Hence, the Peak Repetitive Reverse Voltage ( $V_{RRM}$ ) rating of the diodes must be chosen to be higher than  $2V_m$  to avoid reverse breakdown.

→During its conducting state, each diode has a forward current that is

equal to the load current and, therefore, the Peak Repetitive Forward Current ( $I_{FRM}$ ) rating of these diodes must be chosen to be higher than the peak load current  $V_m/R$  in practice.

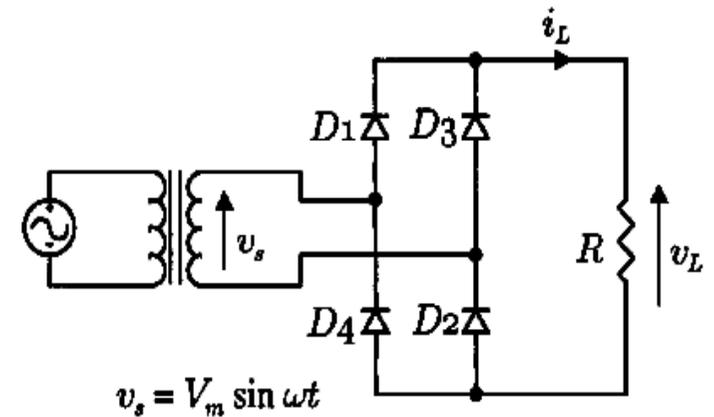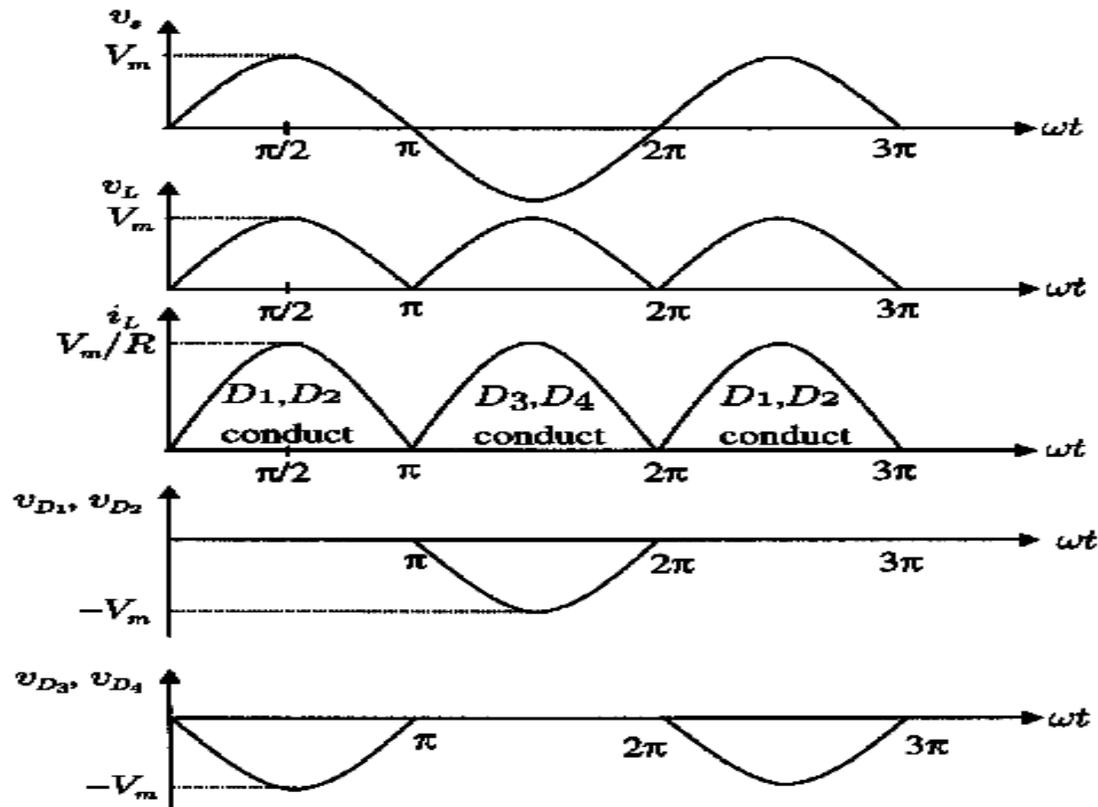**Bridge rectifier:** It can provide full-wave rectification without using a center-tapped transformer. During the positive half cycle of the transformer secondary voltage, the current flows to the load through diodes  $D_1$  and  $D_2$ . During the negative half cycle,  $D_3$  and  $D_4$  conduct.



→As with the full-wave rectifier with center-tapped transformer, the Peak Repetitive Forward Current ( $I_{FRM}$ ) rating of the employed diodes must be chosen to be higher than the peak load current  $V_m = I_m \times R$

→ However, the peak inverse voltage (PIV) of the diodes is reduced from  $2V_m$  to  $V_m$  during their blocking state.

$$V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) = V_m |\sin \omega t| \text{ for both the positive and negative half-cycles. Hence;}$$

Therefore;

$$\text{Full-wave } V_{dc} = \frac{2V_m}{\pi} = 0.636 V_m$$

The root-mean-square (rms) value of load voltage  $v_L$  is  $V_L$ , which is defined as:

$$V_L = \left[ \frac{1}{T} \int_0^T v_L^2(t) dt \right]^{1/2}$$

Hence, the equation can be rewritten as:

$$V_L = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)}$$

OR

$$\text{Full-wave } V_L = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

Therefore; the average and the rms value load current is:

$$I_{dc} = \frac{0.636 V_m}{R}$$

$$I_L = \frac{0.707 V_m}{R}$$

The rectification ratio is:

$$\frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

$$= \frac{(0.636 V_m)^2}{(0.707 V_m)^2} = 81\%$$

The FF can be found by:

$$\mathbf{FF} = \frac{V_L}{V_{dc}} \quad \text{or} \quad \frac{I_L}{I_{dc}}$$

$$\mathbf{FF} = \frac{0.707 V_m}{0.636 V_m} = 1.11$$

The ripple factor (RF), which is a measure of the ripple content, is defined as:

$$\mathbf{RF} = \frac{V_{ac}}{V_{dc}}$$

$$V_{ac} = \sqrt{V_L^2 - V_{dc}^2}$$

$$\mathbf{RF} = \sqrt{\left(\frac{V_L}{V_{dc}}\right)^2 - 1} = \sqrt{\mathbf{FF}^2 - 1}$$

$$\mathbf{RF} = \sqrt{1.11^2 - 1} = 0.482$$