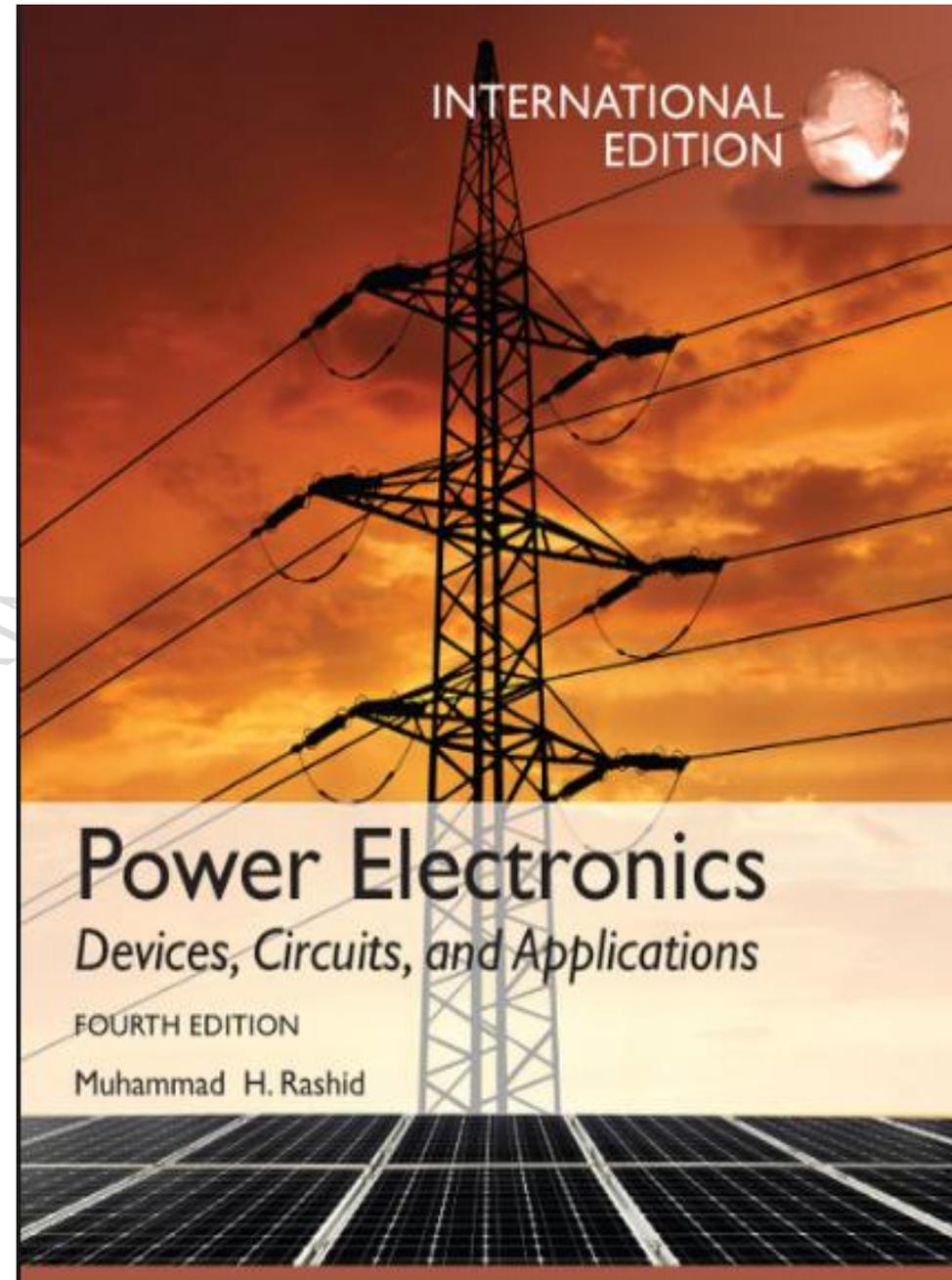


**University of Technology**  
**Laser and Optoelectronic Engineering**  
**Department**  
**Power Electronics/2018-2019)**  
**For the third years (Laser Engineering)**

**Prepared by: Lec. Dr. Mothana Amaar Hassan**  
**Laser and Optoelectronic Engineering**  
**Department**



***Ref: Power Electronics 4<sup>th</sup> edition/ Muhammed H. Rashid***


## Lecture No.8


### Three-Phase Diode Rectifiers

There are two types of three-phase diode rectifier, star rectifiers and bridge rectifiers.
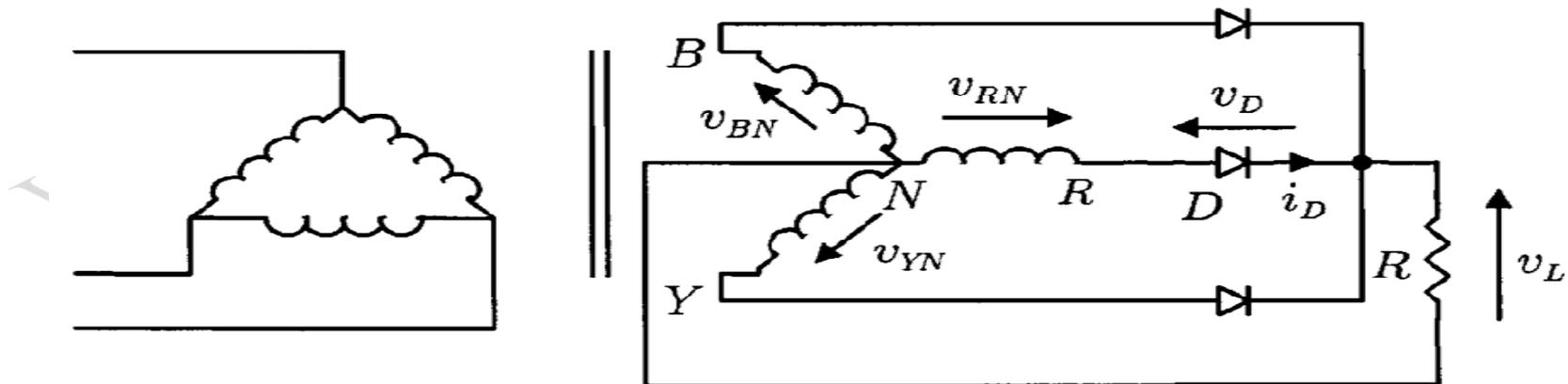
### Three-Phase Star Rectifiers

A basic three-phase star rectifier circuit is shown in Figure below. This circuit can be considered as three single-phase half-wave rectifiers combined together. Therefore, it is sometimes referred to as a three-phase half-wave rectifier. The diode in a particular phase conducts during the period when the voltage on that phase is higher than that on the other two phases.



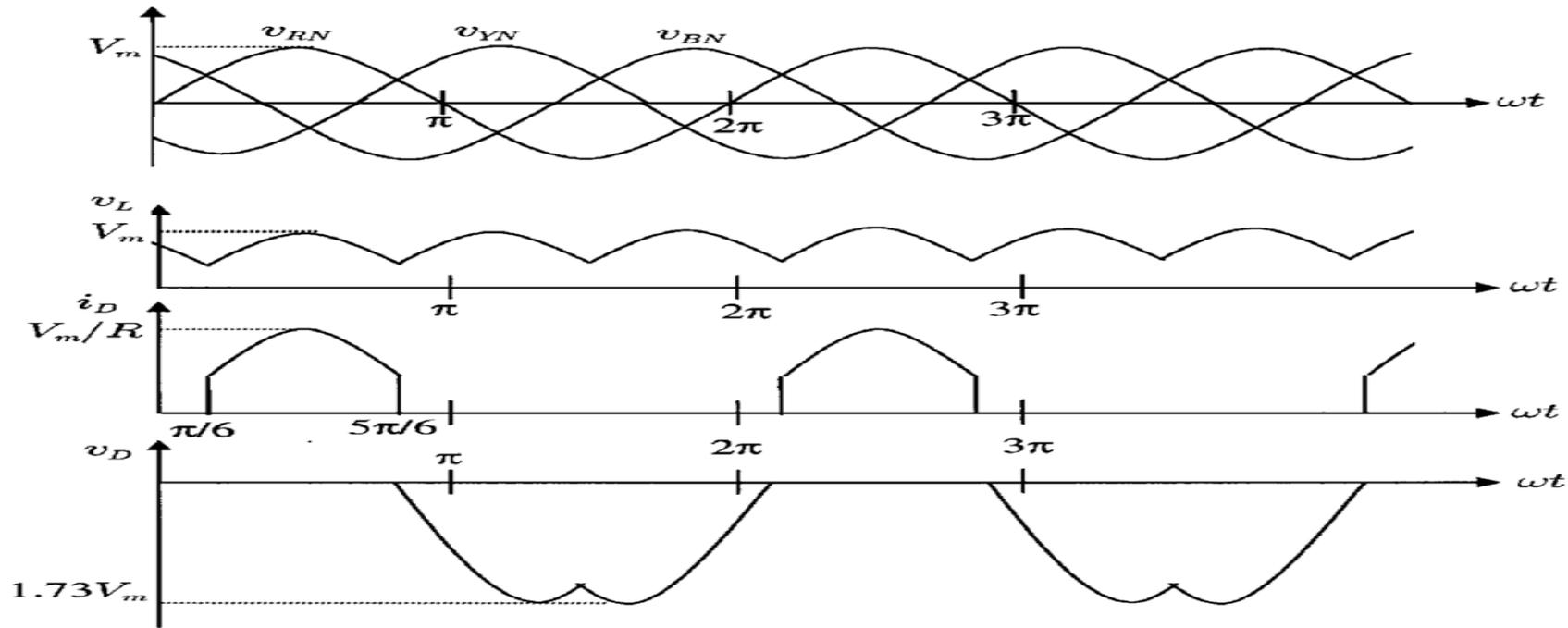

→ It is clear that, unlike the single-phase rectifier circuit, the conduction angle of each diode is  $2\pi/3$ , instead of  $\pi$ .

→ Taking phase R as an example, diode D conducts from  $\pi/6$  to  $5\pi/6$ .

Therefore, the average value of the output can be found as:

$$V_{dc} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin \theta d\theta$$

Or,

$$V_{dc} = V_m \frac{3}{\pi} \frac{\sqrt{3}}{2} = 0.827 V_m$$

Similarly, the rms value of the output voltage can be found as:

$$V_L = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} (V_m \sin \theta)^2 d\theta}$$

Or,

$$V_L = V_m \sqrt{\frac{3}{2\pi} \left( \frac{\pi}{3} + \frac{\sqrt{3}}{4} \right)} = 0.84 V_m$$

The rms current in each transformer secondary winding can also be found as:

$$I_s = I_m \sqrt{\frac{1}{2\pi} \left( \frac{\pi}{3} + \frac{\sqrt{3}}{4} \right)} = 0.485 I_m$$

- It is clear that the peak inverse voltage (PIV) of the diodes is equal to  $1.73V_m$  during their blocking state. Hence, the Peak Repetitive Reverse Voltage ( $V_{RRM}$ ) rating of the diodes must be chosen to be higher than  $1.73V_m$  to avoid reverse breakdown.
- During its conducting state, each diode has a forward current that is equal to the load current and, therefore, the Peak Repetitive Forward Current ( $I_{FRM}$ ) rating of these diodes must be chosen to be higher than the peak load current  $I_m = V_m \times R$  in practice.

→ Form factor of diode current  $I_s / I_{dc} = 1.76$

→ The rectification ratio is:

$$\frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

$$FF = \frac{V_L}{V_{dc}} \quad \text{or} \quad \frac{I_L}{I_{dc}}$$

→ Form factor of three-phase half-wave rectifier

$$FF = \frac{0.84V_m}{0.827V_m} = 1.0165$$

→ Ripple factor of three-phase half-wave rectifier

$$\begin{aligned}\text{RF} &= \sqrt{\left(\frac{V_L}{V_{dc}}\right)^2 - 1} = \sqrt{\text{FF}^2 - 1} \\ &= 0.182\end{aligned}$$

LASER ENGINEERING BRANCH